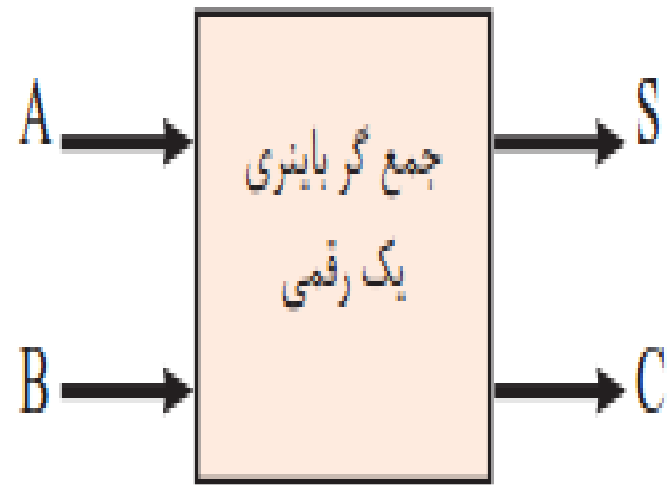


آزمایشگاه سیستم های دیجیتال 2

آزمایش 2


جمع کننده ها

## نیمه جمع کننده (Half adder)




A	B	C	S	
0	0	0	0	$0 + 0 = 0$
0	1	0	1	$0 + 1 = 1$
1	0	0	1	$1 + 0 = 1$
1	1	1	0	$1 + 1 = 10$



# تمام جمع کننده (Full adder)

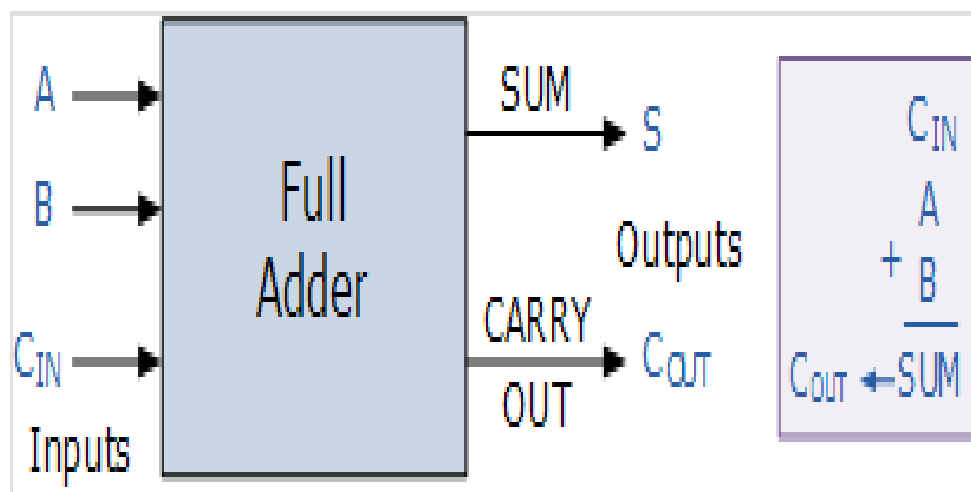

C-in	B	A	Sum	C-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

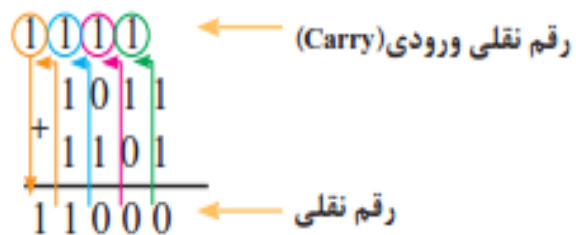


ادامه

  

# Gate Level Logic

## Gate Primitives

### Majority Circuit

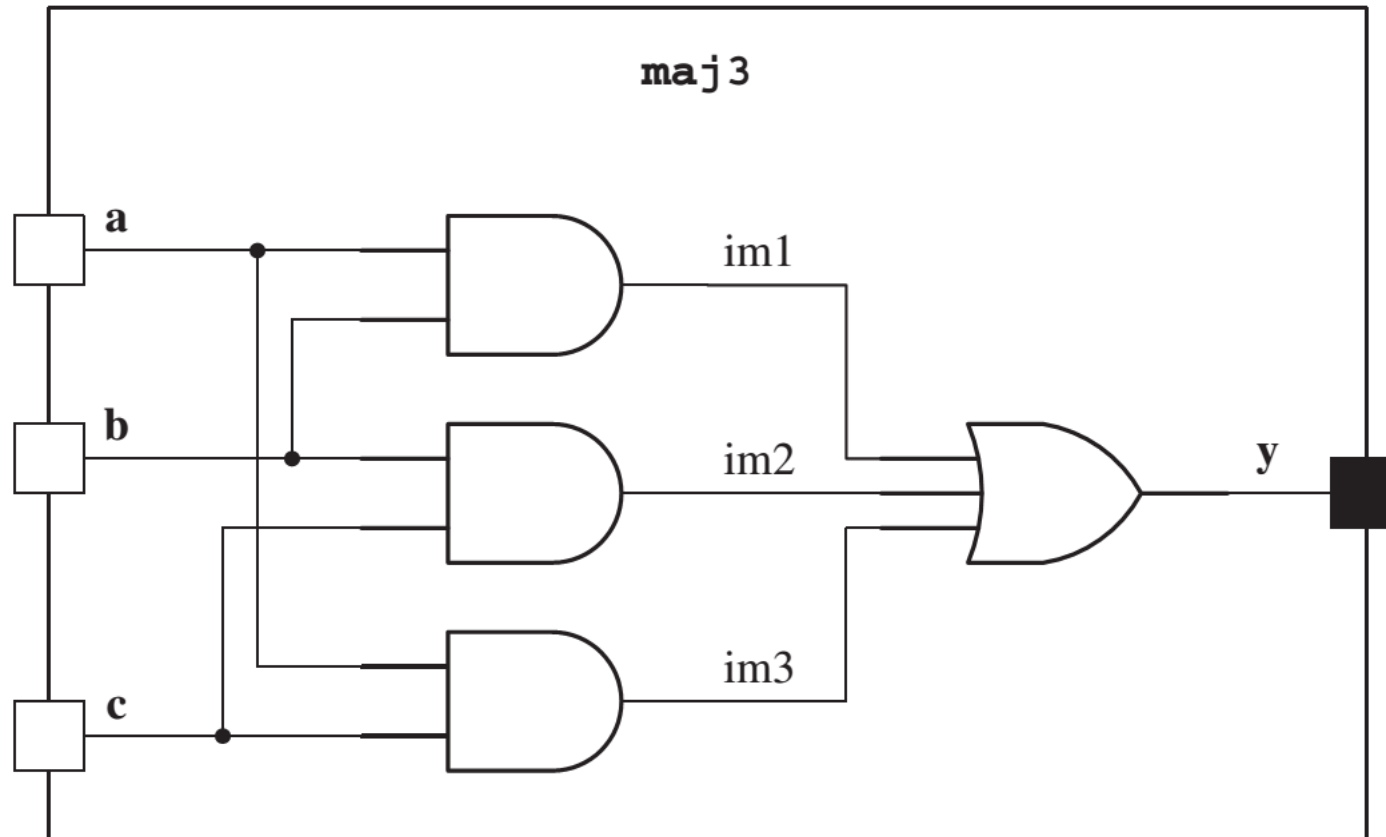

# Gate Level Logic

## Gate Primitives

### Majority Circuit

```
module maj3 (a, b, c, y);  
    input a, b, c;  
    output y;  
    wire im1, im2, im3;  
  
    and #(2, 4)  
        ( im1, a, b ),  
        ( im2, b, c ),  
        ( im3, c, a );  
    or #(3, 5) (y, im1, im2, im3);  
  
endmodule
```

# Assign Statements

## Bitwise operators

### maj3 with assign Statement

```
`timescale 1ns/100ps
```

```
module maj3 (input a, b, c, output y);  
    assign #(4) y = ( a & b ) | ( b & c ) | ( a & c );  
endmodule
```

# Gate Level Logic

## Gate Primitives

### Test for Majority Circuit

```
module test_maj;
    // Inputs
    reg a;
    reg b;
    reg c;
    // Outputs
    wire y;
    // Instantiate the Unit Under Test (UUT)
    maj3 uut (
        .a(a),
        .b(b),
        .c(c),
        .y(y));
endmodule
```


```
initial begin
    // Initialize Inputs
    a = 0; b = 0; c = 0;
    #20 a = 1;
    #5 b = 1;
    #20 a = 0; b = 0; c = 0;
    #20 a = 1;
    #5 c = 1;
    #20 a = 0; b = 0; c = 0;
    #20 b = 1;
    #5 c = 1;
    #20 a = 0; b = 0; c = 0;
end
endmodule
```



# Gate Level Logic

## Three input XOR

### XOR Circuit

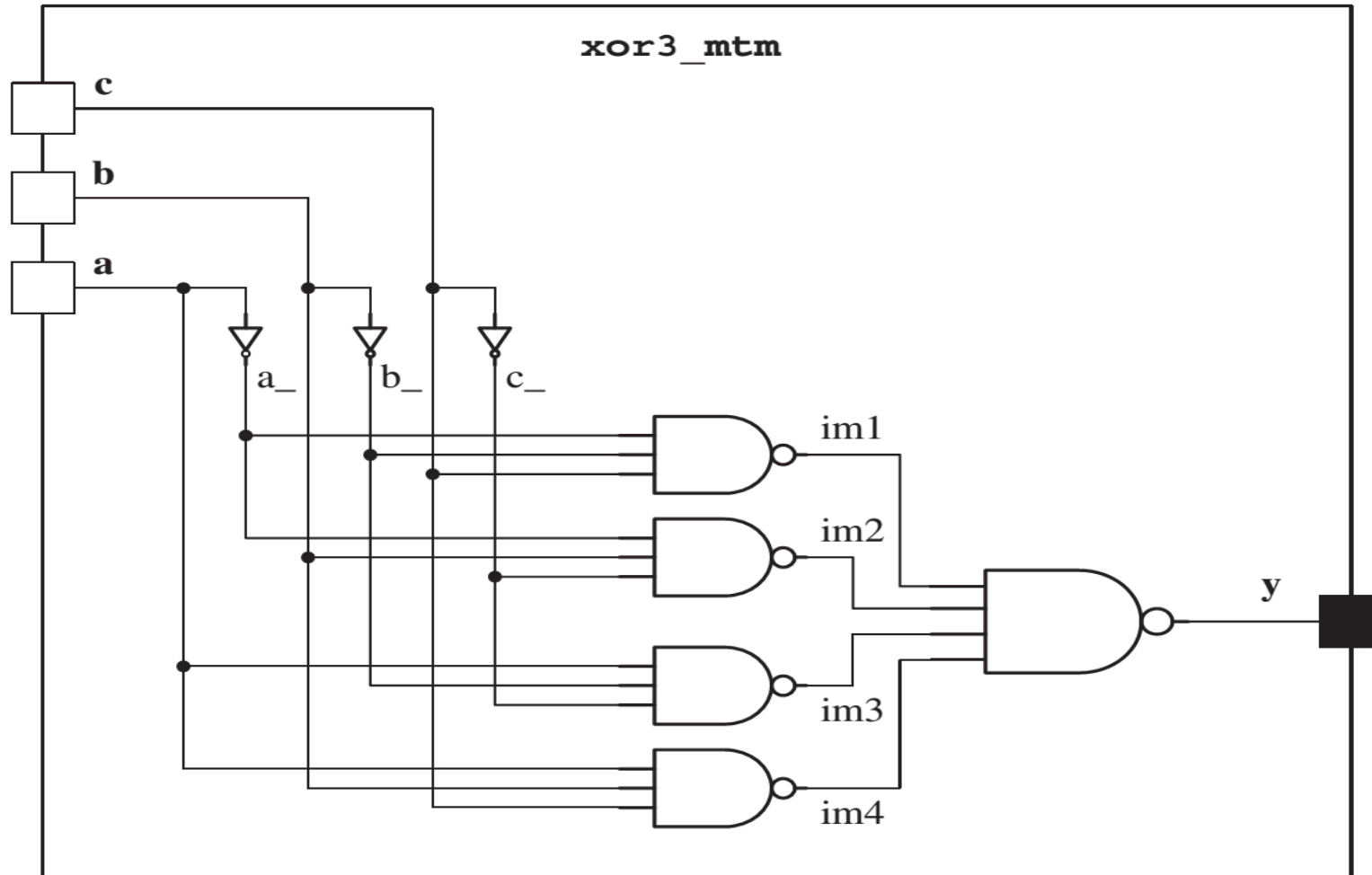

# Gate Level Logic

## Three input XOR XOR Circuit

```
module xor3_mtm (input a, b, c, output y);  
  wire a_, b_, c_;  
  wire im1, im2, im3, im4;  
  
  not #(1:3:5, 2:4:6)  
    ( a_, a ),  
    ( b_, b ),  
    ( c_, c );  
  nand #(2:4:6, 3:5:7)  
    ( im1, a_, b_, c ),  
    ( im2, a_, b, c_ ),  
    ( im3, a, b_, c_ ),  
    ( im4, a, b, c );  
  nand #(2:4:6, 3:5:7) (y, im1, im2, im3, im4);  
  
endmodule
```

Min : type : Max Delay

# Assign Statements

## Bitwise operators

### xor3 with assign Statement

```
`timescale 1ns/100ps

module xor3 (input a, b, c, output y);
    assign y = a ^ b ^ c;
endmodule
```

# Gate Level Logic

## Three input XOR

### Test for XOR Circuit

```
module test_xor3;

    // Inputs
    reg a;
    reg b;
    reg c;

    // Outputs
    wire y;

    // Instantiate the Unit Under Test (UUT)
    xor3_mtm uut (
        .a(a),
        .b(b),
        .c(c),
        .y(y)
    );

    initial repeat (9) #10 a = ~a;
    initial repeat (5) #20 b = ~b;
    initial repeat (5) #40 c = ~c;
    initial begin
        // Initialize Inputs
        a = 0;
        b = 0;
        c = 0;

        // Wait 100 ns for global reset to finish
        #100;


        // Add stimulus here

    end
end
```

# Hierarchical Structures

## Simple hierarchies

### Full Adder Using xor3\_p and maj3\_p

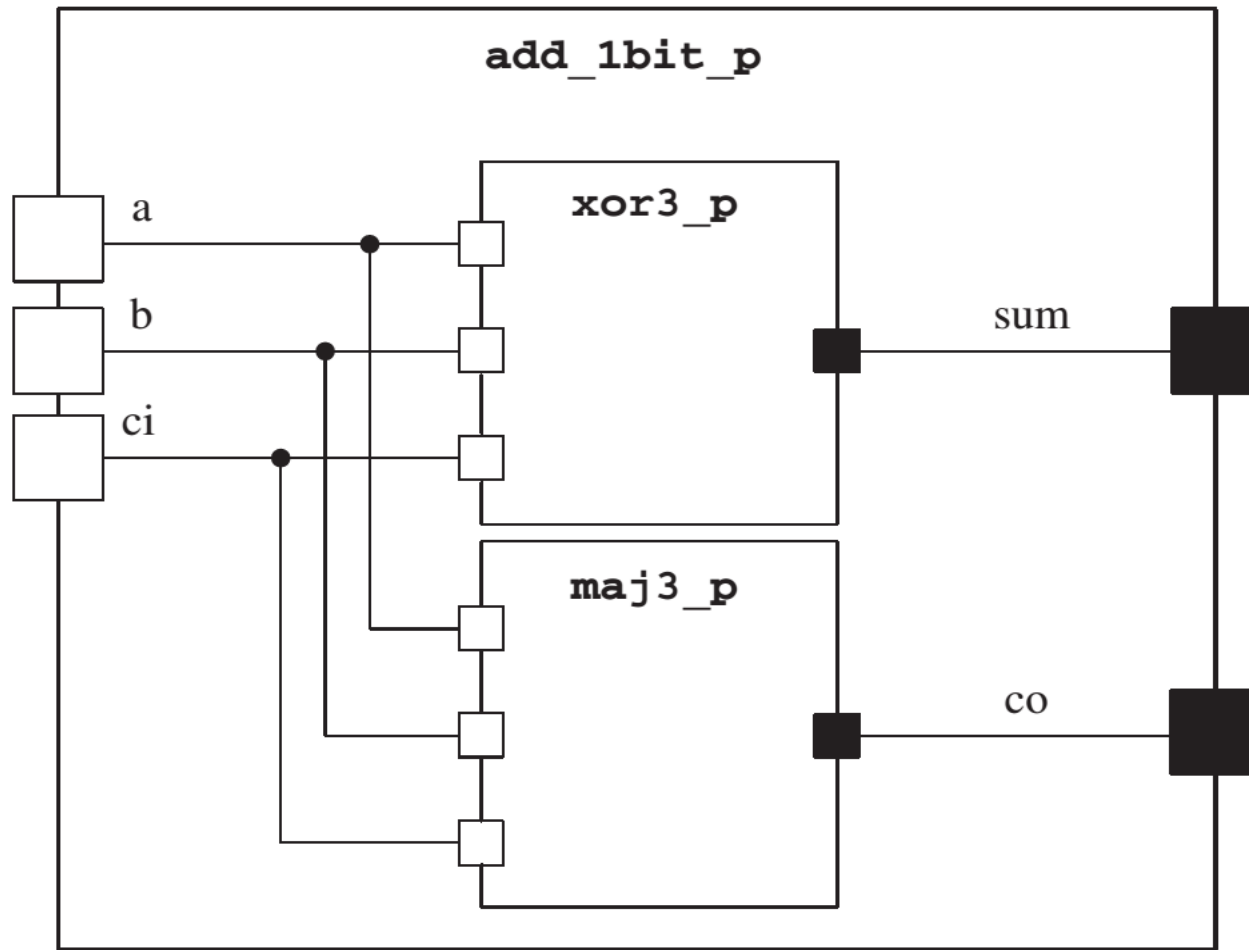

# Assign Statements

## Bitwise operators

### Add 1 bit with assign Statement

```
`timescale 1ns/100ps

module add_1bit (input a, b, ci, output s, co);

    assign #(10) s = a ^ b ^ ci;
    assign #(8) co = ( a & b ) | ( b & ci ) | ( a & ci );

endmodule
```

# Assign Statements

## Bitwise operators

### Full Adder Using Concatenation

```
`timescale 1ns/100ps

module add_1bit (input a, b, ci, output s, co);
    assign #(3, 4) {co, s} = {(a & b) | (b & ci) | (a & ci), a^b^ci};
endmodule
```

# Hierarchical Structures

## Simple hierarchies

### Full Adder Using xor3\_p and maj3\_p

```
`timescale 1ns/100ps

module add_1bit_p (input a, b, ci, output sum, co);

    xor3_p xr1 (a, b, ci, sum);
    maj3_p mj1 (a, b, ci, co);

endmodule
```



# Hierarchical Structures

## Simple hierarchies

### Test for Full Adder Using xor3\_p and maj3\_p

```
module test_1bit_p;
    // Inputs
    reg a;
    reg b;
    reg ci;
    // Outputs
    wire s;
    wire co;
    // Instantiate the Unit Under Test (UUT)
    add_1bit_p uut (
        .a(a),
        .b(b),
        .ci(ci),
        .sum(s),
        .co(co));
endmodule
```


```
initial begin
    // Initialize Inputs
    a = 0;
    b = 0;
    ci = 0;
    #50 a = 1;
    #50 b = 1;
    #50 ci = 1;
    #50 a = 0;
    #50 b = 0;
    // Wait 100 ns for global reset to finish
    #100;
    // Add stimulus here

end
endmodule
```

# Hierarchical Structures

## Vector declarations
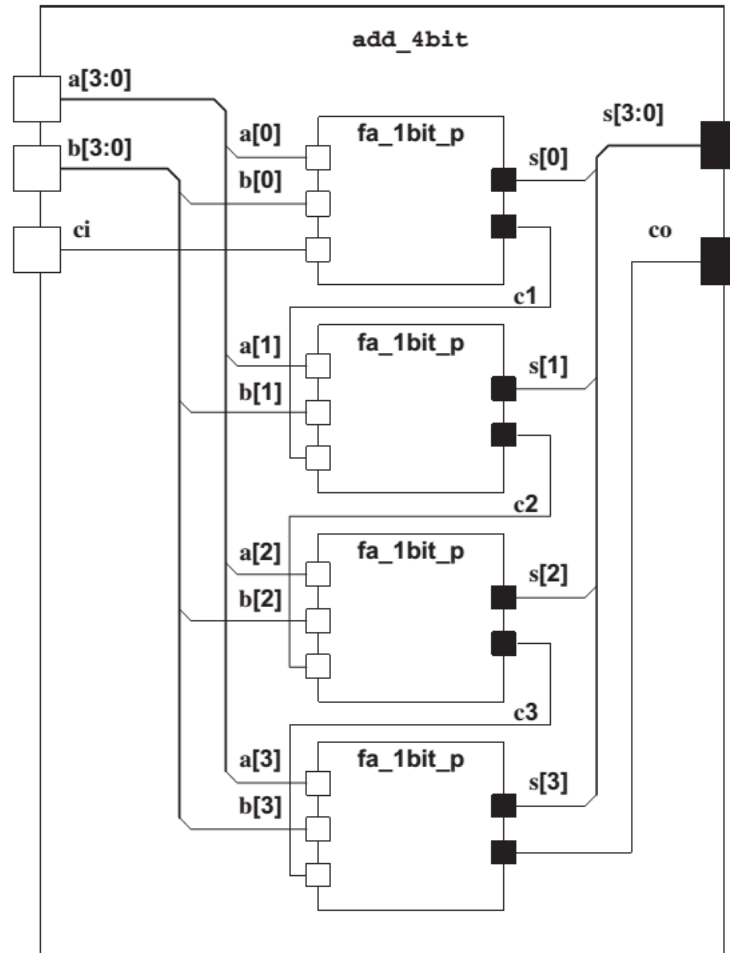
### A 4-bit Adder by Wiring Four Full Adders



# Hierarchical Structures

## Vector declarations

### A 4-bit Adder by Wiring Four Full Adders

```
`timescale 1ns/100ps
```

```
module add_4bit (input [3:0] a, b, input ci,  
                output [3:0] s, output co);  
  wire c1, c2, c3;
```

```
  add_1bit_p fa0 (a[0], b[0], ci, s[0], c1);  
  add_1bit_p fa1 (a[1], b[1], c1, s[1], c2);  
  add_1bit_p fa2 (a[2], b[2], c2, s[2], c3);  
  add_1bit_p fa3 (a[3], b[3], c3, s[3], co);
```

```
endmodule
```

OR

```
add_1bit_p fa1 (.a(a[1]),.b(b[1]),.ci(c1),.sum(s[1]),.co(c2));
```

# Hierarchical Structures

## Iterative structures

### 4-bit Adder Using Array of Instances

```
`timescale 1ns/100ps

module add_4bit_vec (input [3:0] a, b, input ci,
                    output [3:0] s, output co);
    wire c1, c2, c3;
    add_1bit_p fa[3:0] (a, b, {c3, c2, c1, ci}, s,
                       {co, c3, c2, c1});

endmodule
```

# Hierarchical Structures

## Vector declarations

### A 4-bit Adder by Wiring Four Full Adders

```
module test_add4;
    // Inputs
    reg [3:0] a;
    reg [3:0] b;
    reg ci;
    // Outputs
    wire [3:0] s;
    wire co;
    // Instantiate the Unit Under Test (UUT)
    add_4bit uut (
        .a(a),
        .b(b),
        .ci(ci),
        .s(s),
        .co(co));
endmodule
```

```
initial begin
    // Initialize Inputs
    a = 0;
    b = 0;
    ci = 0;
    #50 a = 4'b1010; b = 4'b1001;
    #50 a = 4'b0010; b = 4'b1001;
    #50 a = 4'b1011; b = 4'b1101; ci = 1;
    // Wait 100 ns for global reset to finish
    #100;
    // Add stimulus here

end
endmodule
```