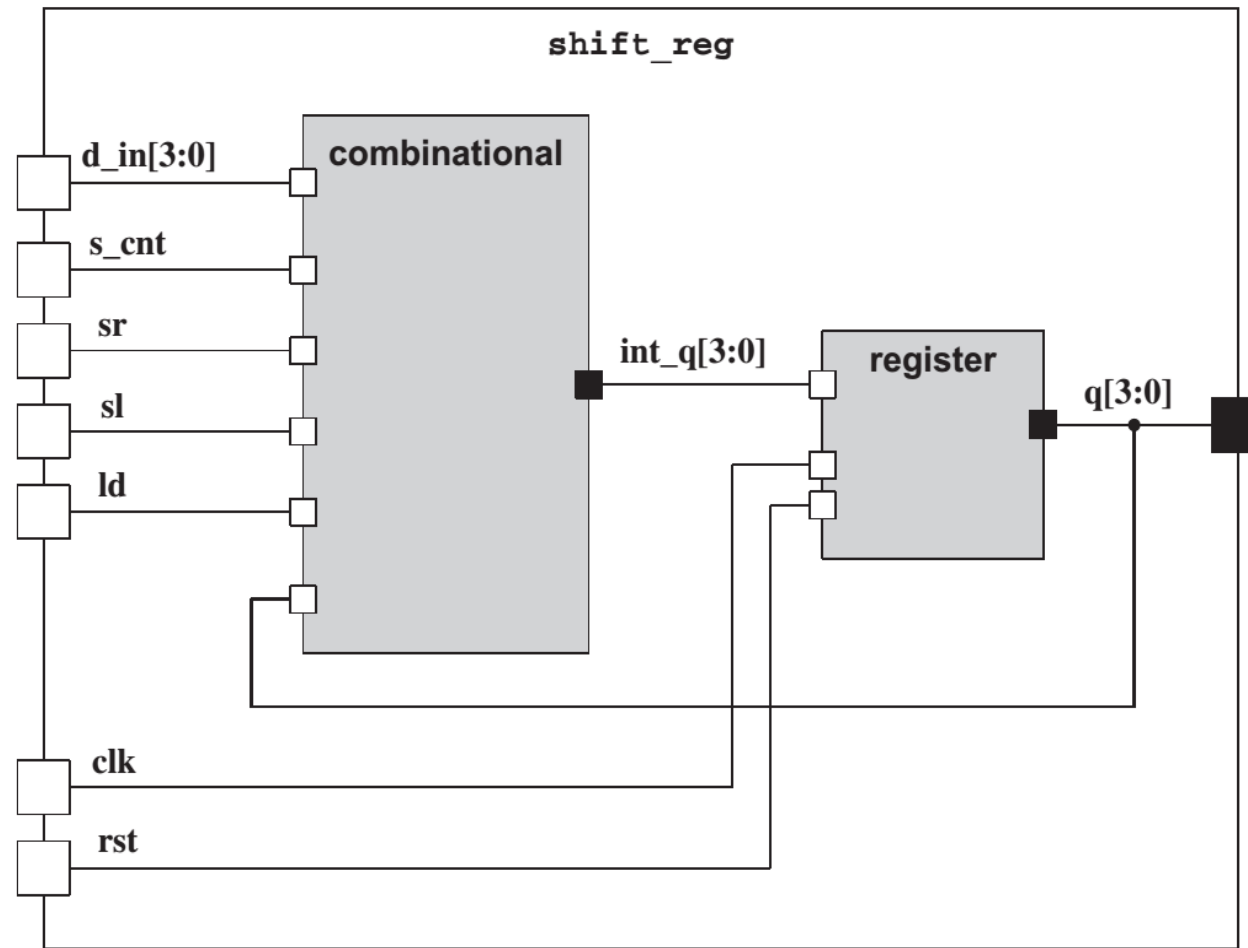


Sequential Circuit Description

Separate register & combinational blocks

Multi-bit Shifter with Separate Register Block



Sequential Circuit Description

Separate register & combinational blocks

Shifter Verilog Code


```
module shift_reg( input [3:0] d_in, input clk, sr, sl, ld, rst,
                  input [1:0] s_cnt, output reg [3:0] q);
    reg [3:0] int_q;
    always @( d_in, q, s_cnt, sr, sl, ld ) begin: combinational
        if( ld )
            int_q = d_in;
        else if( sr )
            int_q = q >> s_cnt;
        else if( sl )
            int_q = q << s_cnt;
        else int_q = q;
    end
    always @( posedge clk ) begin: register
        if (rst) q <= 0;
        else q <= int_q;
    end
endmodule
```

آزمایشگاه سیستم های دیجیتال 2



آزمایش 5

مالتی پلکسر - دی مالتی پلکسر

Multiplexer



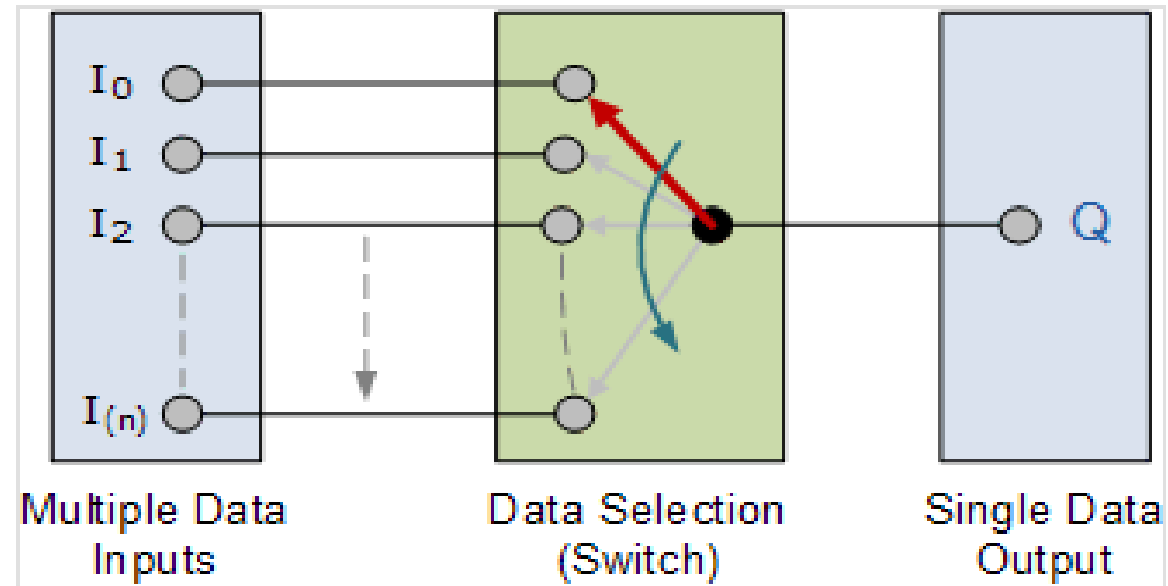


Continued

  


s	out
0	I_0
1	I_1

Continued

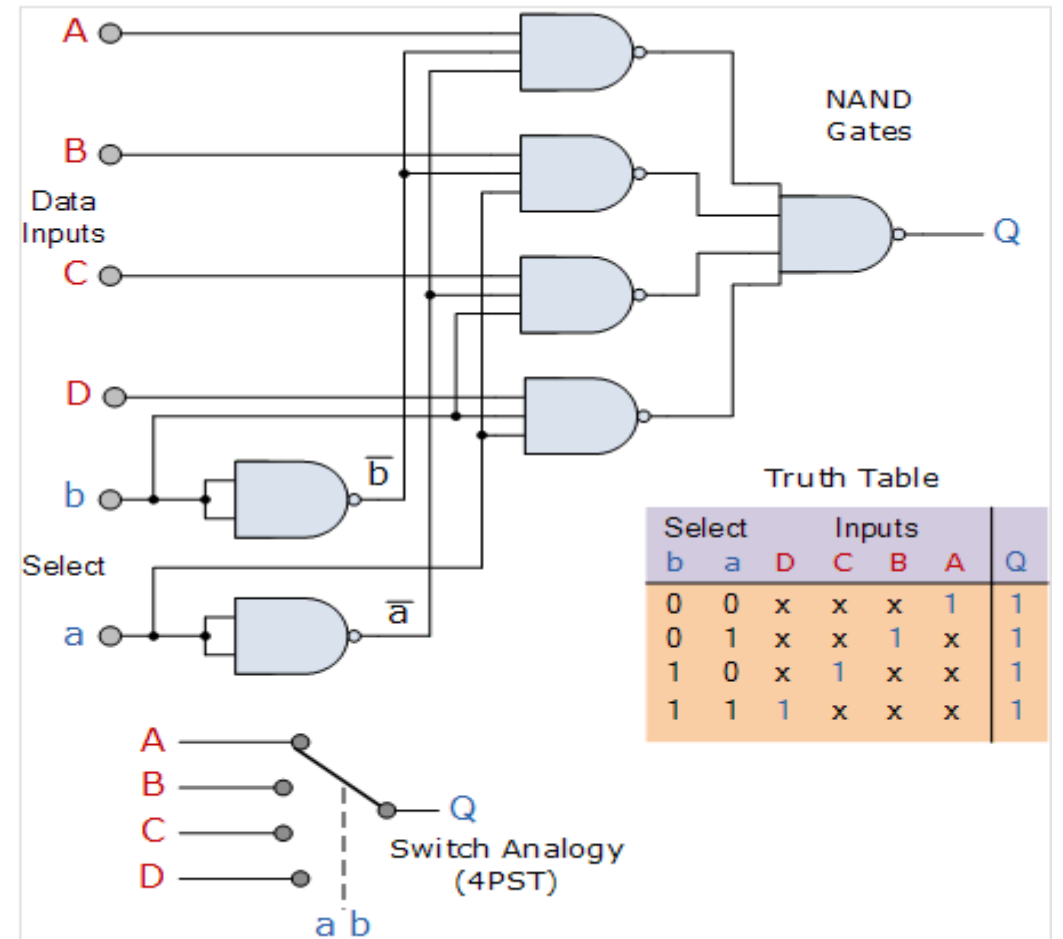  


Continued

 

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

Register Transfer Level Design with Verilog

A Multiplexer Using Basic Gates

 

Register Transfer Level Design with Verilog

A Multiplexer Using Basic Gates

Primitive instantiations

```
module MultiplexerA (input a, b, s, output w);  
    wire a_sel, b_sel, s_bar;  
    not U1 (s_bar, s);  
    and U2 (a_sel, a, s_bar);  
    and U3 (b_sel, b, s);  
    or U4 (w, a_sel, b_sel);  
endmodule
```

Register Transfer Level Design with Verilog

A Multiplexer

Assign Statement and Boolean

```
module MultiplexerB (input a, b, s, output w);  
    assign w = (a & ~s) | (b & s);  
endmodule
```

Register Transfer Level Design with Verilog

A Multiplexer

Assign Statement and Condition operator

```
module MultiplexerC (input a, b, s, output w);  
    assign w = s ? b : a;  
endmodule
```



Register Transfer Level Design with Verilog


A Multiplexer

Procedural Statement

```
module MultiplexerD (input a, b, s, output w);  
    reg w;  
    always @ (a, b, s) begin  
        if (s) w = b;  
        else w = a;  
    end  
endmodule
```

Register Transfer Level Design with Verilog

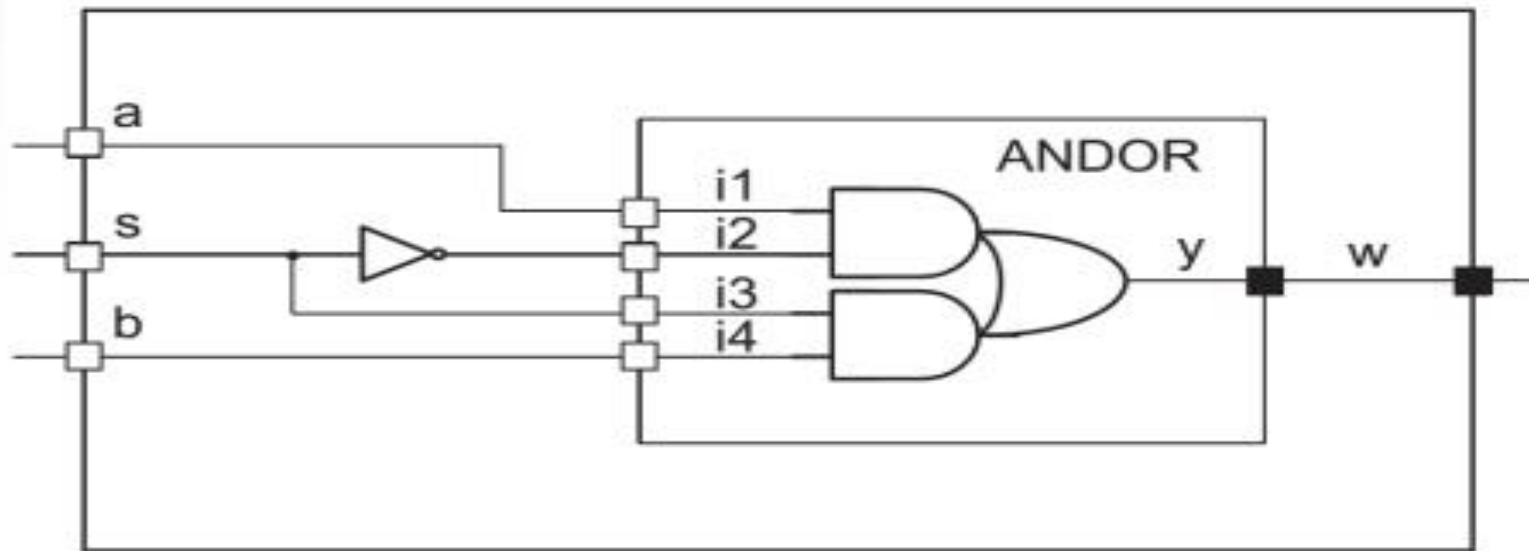A Multiplexer Using ANDOR Module Instantiation



Register Transfer Level Design with Verilog

A Multiplexer Using ANDOR Module Instantiation

```
module ANDOR (input i1, i2, i3, i4, output y);  
    assign y = (i1 & i2) | (i3 & i4);  
endmodule  
  
//  
module MultiplexerE (input a, b, s, output w);  
    wire s_bar;  
    not U1 (s_bar, s);  
    ANDOR U2 (a, s_bar, s, b, w);  
endmodule
```


Register Transfer Level Design with Verilog

A Multiplexer

Test bench for all Multiplexer

```
module test(output w);  
    reg a,s=0,b;  
    //wire w;  
    MultiplexerA ic1 (a,s,b,w);  
    always  
    begin  
        #20; s = ~s;  
    end  
  
    initial  
    begin  
        #10; a = 1; b = 0;  
        #50; a = 0; b = 1;  
        #200; $stop;  
    end  
  
endmodule
```